
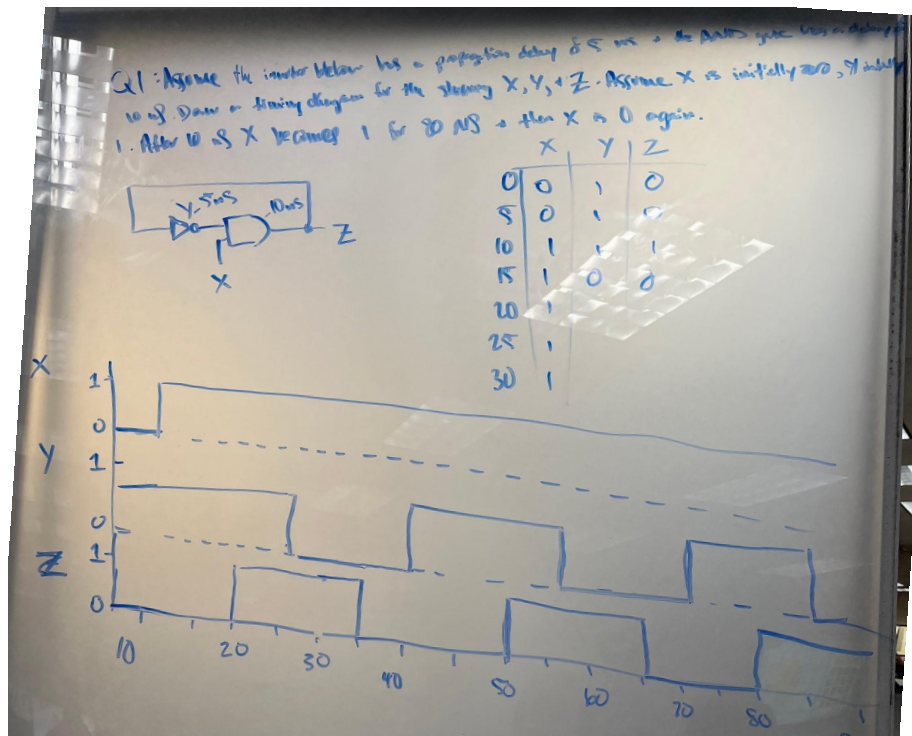



(1)

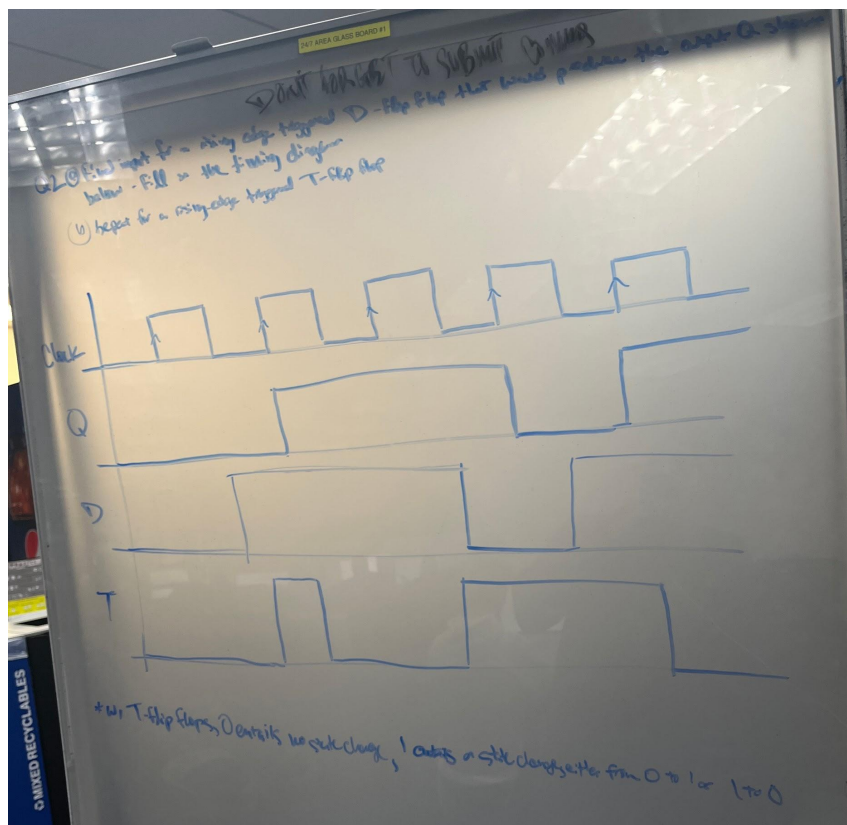


(2)



(3)

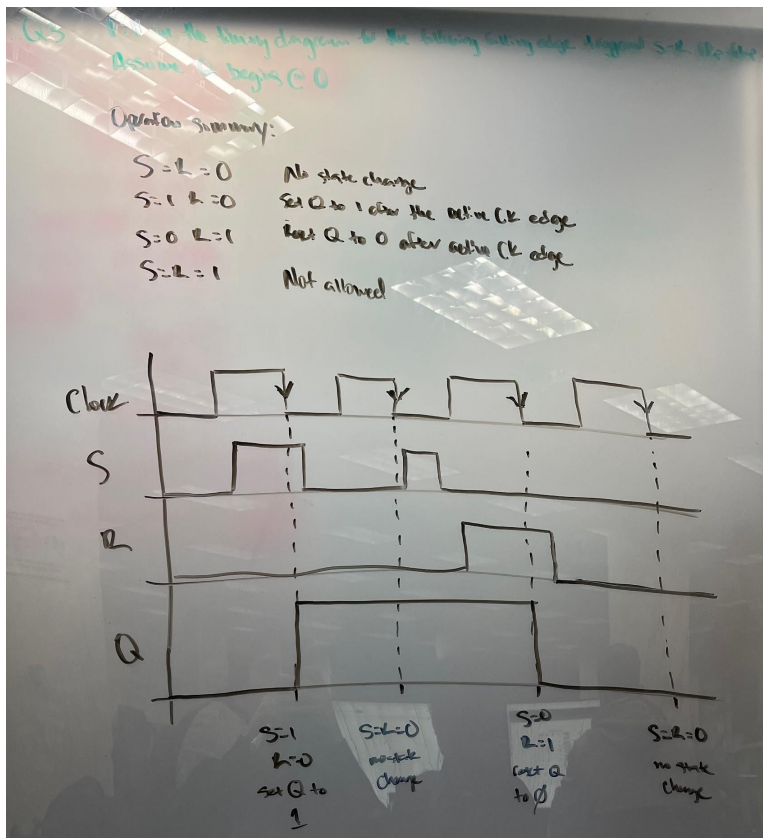


(4)

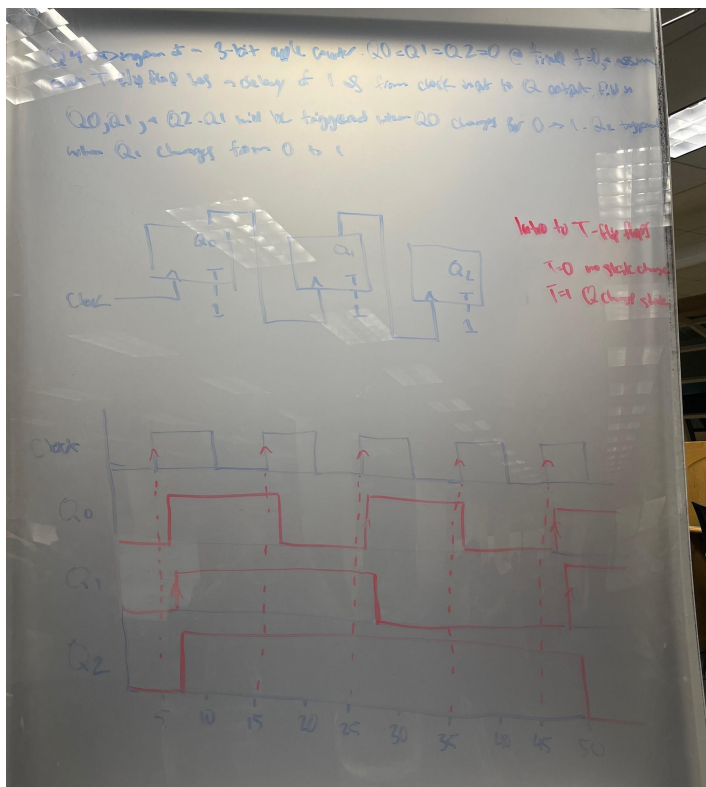


(5)

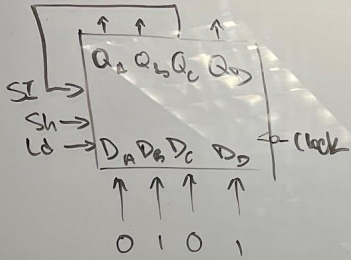Q5: 74178 Shift register is described by the given table. All state changes occur on the 1-0 transition (falling edge) of the clock. Shift register is connected as shown. Complete the timing diagram.




Sh	Ld	Q_A^+	Q_B^+	Q_C^+	Q_D^+
0	0	Q_A	Q_B	Q_C	Q_D
0	1	D_A	D_B	D_C	D_D
1	X	SI	Q_A	Q_B	Q_C

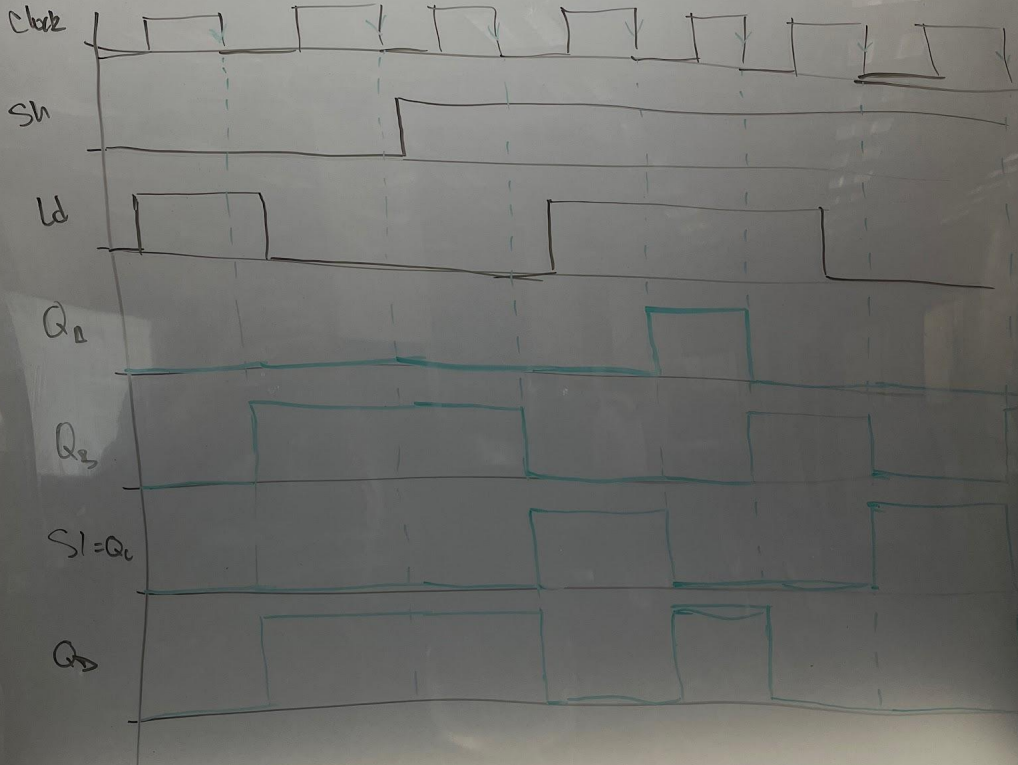

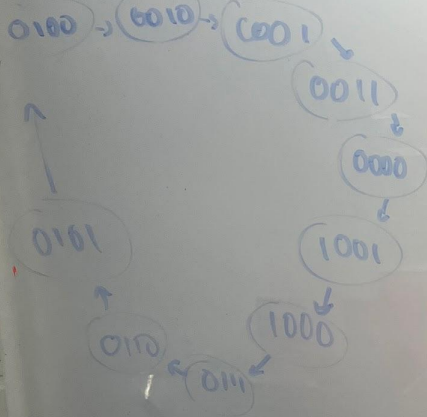(6)

Design a decade counter that counts in the following sequence using D flip-flops:

0100, 0010, 0001, 0011, 0000, 1001, 1000, 0111, 0110, 0101, (repeating) 0100



Next State Table

Present					Next State			
A	B	C	D		A ⁺	B ⁺	C ⁺	D ⁺
0	1	0	0		0	0	1	0
0	0	1	0	✓	0	0	0	1
0	0	0	1	✓	0	0	1	1
0	0	1	1		0	0	0	0
0	0	0	0	✓	1	0	0	1
1	0	0	1		1	0	0	0
1	0	0	0	✓	0	1	1	1
1	0	1	1		0	1	1	0
1	0	1	0		0	1	0	1
1	0	0	1		0	1	0	0

A⁺

AB	00	01	11	10
CD	00	1		
01				1
11				
10				

$$A^+ = A'B'C'D' + A'BC'D$$

B⁺

AB	00	01	11	10
CD	00			1
01		1		
11		1		
10			1	

$$B^+ = A'BD + A'BC + A'CD$$

C⁺

AB	00	01	11	10
CD	00	1		1
01	1			
11			1	
10				

$$C^+ = A'BC'D' + A'BC'D + A'BC'D + A'BC'D$$

D⁺

AB	00	01	11	10
CD	00	1		
01		1		
11				1
10				


$$D^+ = A'BC'D' + A'BC'D + A'BC'D + A'BC'D$$

$$A^+ = A'B'C'D' + AB'C'D$$

$$B^+ = A'BD + ABC + AB'C'D'$$

$$C^+ = A'BC'D' + AB'C'D' + AB'C'D + A'BCD$$

$$D^+ = B'C'D' + A'B'C' + A'CD'$$

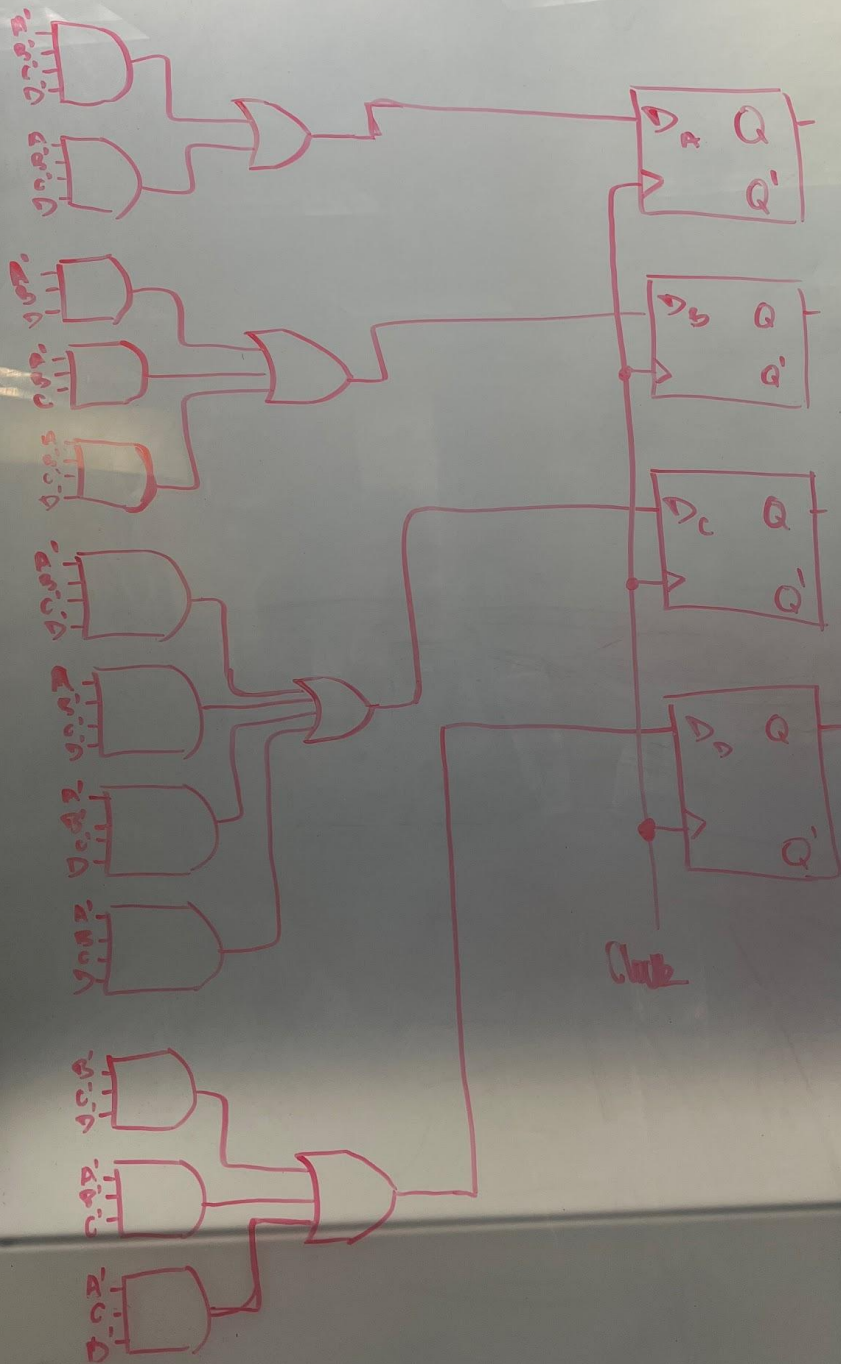

(7)

Q7. Design a circuit using D flip-flops that will generate the sequence 001, 011, 101, 110, 001, ... repeat. Do this by designing - Counter for any sequence of states. See that the 1st flip-flop takes as this sequence. Don't duplicate states bc each state can only have 1 next state.

$A^+ = C'A'$


Present			Next		
C	B	A	A ⁺	B ⁺	C ⁺
0	0	0	0	0	1
0	0	1	1	0	0
1	0	0	0	1	0
0	1	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

$C^+ = B'A + CBA$

C	B	A	C ⁺
0	0	0	1
0	0	1	0
1	0	0	0
0	1	0	1
1	0	1	0
1	1	0	0

$B^+ = CB'$

C	B	A	B ⁺
0	0	0	0
0	0	1	0
1	0	0	0
0	1	0	1
1	0	1	0
1	1	0	0

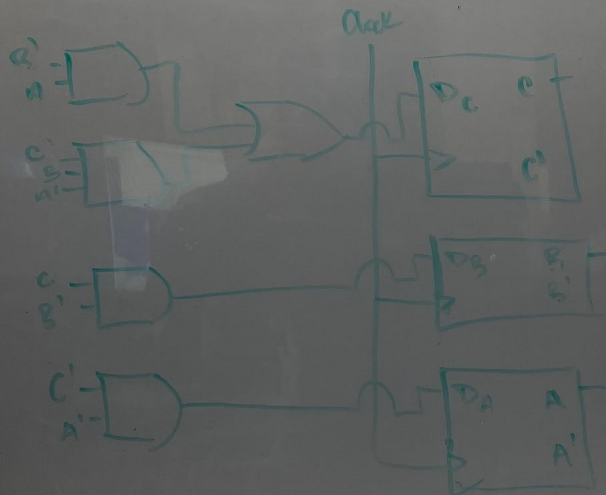

(8)

Q8: Design a decade counter which counts from 0-9 using the next 3-state for decimal digit

Decimal	Excess-3	Present State				Next State			
		A	B	C	D	A ⁺	B ⁺	C ⁺	D ⁺
0	0011	0	0	1	1	0	1	0	0
1	0100	0	1	0	0	0	1	0	1
2	0101	0	1	0	1	0	1	1	0
3	0110	0	1	1	0	0	1	1	1
4	0111	1	0	0	0	1	0	0	1
5	1000	1	0	0	1	1	0	1	0
6	1001	1	0	1	0	1	0	1	1
7	1010	1	0	1	1	1	1	0	0
8	1011	1	1	0	0	0	0	1	1
9	1100								

A⁺

AB	00	01	11	10
00				
01				
11			1	
10				

$$A^+ = AB^+ + A'B^+C^+D^+$$

B⁺

AB	00	01	11	10
00				
01		1		
11			1	
10				1

$$B^+ = A'B^+D^+ + A'B^+C^+ + B^+C^+D^+$$

C⁺

AB	00	01	11	10
00			1	
01		1		1
11				
10		1		1

$$C^+ = ABC^+D^+ + A'B^+C^+D^+ + A'B^+C^+D^+ + A'B^+C^+D^+$$

D⁺

AB	00	01	11	10
00		1	1	1
01				
11				
10		1		1

$$D^+ = AB^+D^+ + AC^+D^+ + A'B^+D^+$$

$$A^+ = AB' + A'BCD \checkmark$$

$$B^+ = A'BD' + A'BC' + B'CD$$

$$C^+ = ABC'D + A'BCD + ABC'D + A'BCD' + AB'CD'$$

$$D^+ = AB'D' + ACD' + A'BD'$$

