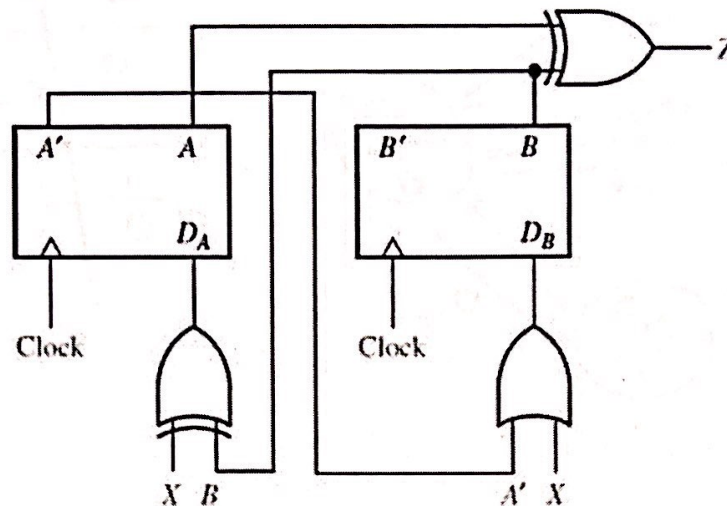


Homework 12-13

First Name:
Last Name:
Red ID#:

12.1

Derive the equations of next state A^+B^+ and output Z as a function of A,B,X for the following circuit:



$$A^+ = D_A = X \oplus B$$

$$B^+ = D_B = A' + X$$


$$Z = B \oplus A$$

12.2

Fill up the next state table (truth table) and draw the state graph of the sequential circuit in 12.1. Is it a Moore circuit or Mealy circuit? Justify your answer.


STATE TABLE

Present State AB	Next State		Z
	x=0	x=1	
00 (S_0)	01 S_1	11 S_3	0
01 (S_1)	11 S_3	01 S_1	1
10 (S_2)	00 S_0	11 S_3	1
11 (S_3)	10 S_2	01 S_1	0

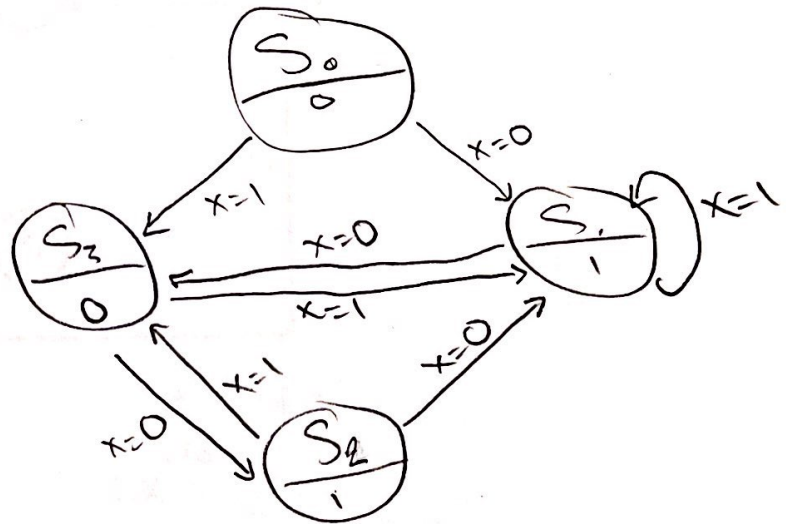

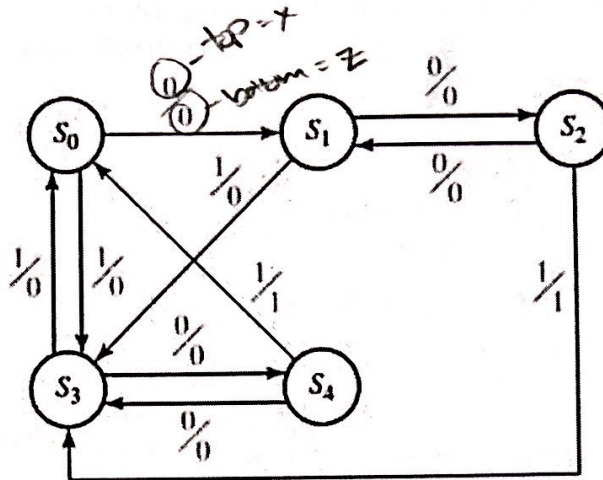12.3

Fill up the next state table and derive the next state equations for the following state graph:



ABX
0110
AXBC
00 11

Present State ABC	Next State $A^+ B^+ C^+$		Z	
	X=0	X=1	X=0	X=1
S_0 (000)	S_1 (001)	S_3 (011)	0	0
S_1 (001)	S_2 (010)	S_3 (011)	0	0
S_2 (010)	S_1 (001)	S_3 (011)	0	1
S_3 (011)	S_4 (100)	S_0 (000)	0	0
S_4 (100)	S_3 (011)	S_0 (000)	0	1
101	xxx	xxx	x	x
110	xxx	xxx	x	x
111	xxx	xxx	x	x

$$A^+ = BCX'$$

CX	AB			
	00	01	11	10
00			x	
01			x	
11			x	x
10		1	x	x

$$B^+ = AX' + A'C'X + B'C$$

CX	AB			
	00	01	11	10
00			x	1
01	1	1	x	
10	1		x	x
11	1		x	x

$$C^+ = C'X' + A'C' + A'B'X$$

CX	AB			
	00	01	11	10
00	1	1	x	1
01	1	1	x	
11	1		x	x
10			x	x

CX	AB			
	00	01	11	10
00			x	
01			x	
11			x	x
10			x	x


$$Z = BC'X + AX$$

* remember to plug
in the x

12.4

Realize the sequential circuit that performs the function specified in the state graph of

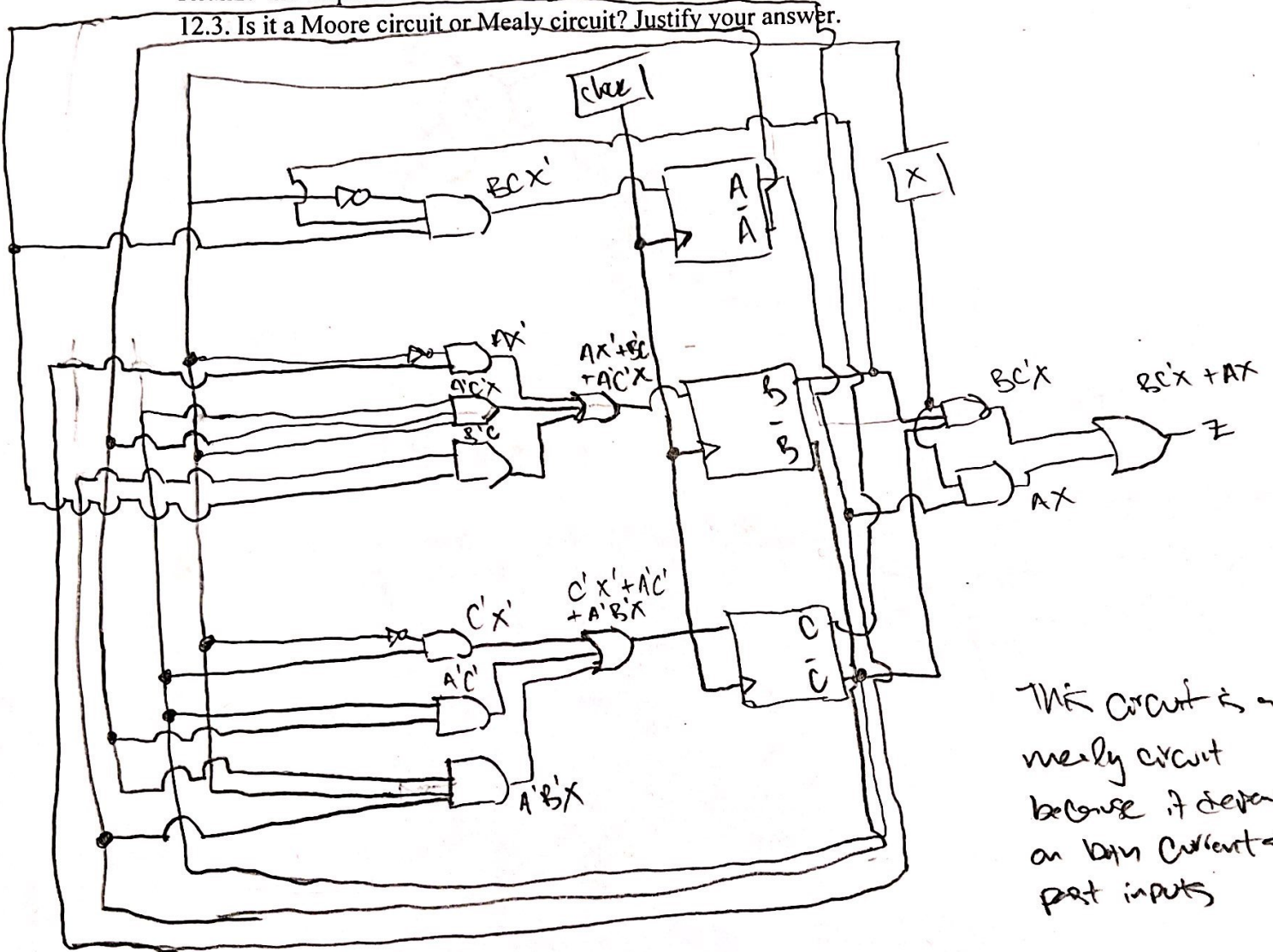
12.3. Is it a Moore circuit or Mealy circuit? Justify your answer.



This circuit is a
mealy circuit
because it depends
on both current
past inputs

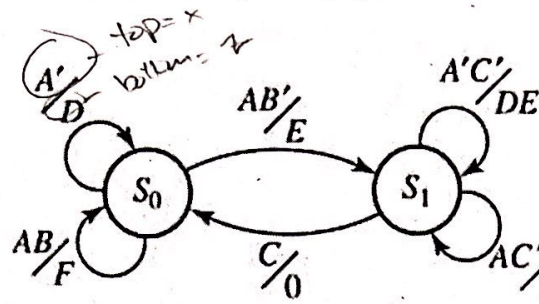13.1

Construct the state table for the following state graph:



Current State	Next State (AB)	Output (DEF)
S_0	S_0	100
S_0	S_0	100
S_0	S_0	100
S_0	S_1	100
S_0	S_1	100
S_0	S_1	100
S_0	S_0	100
S_1	S_0	110
S_1	S_0	110
S_1	S_0	110
S_1	S_1	110
S_1	S_1	110
S_1	S_1	110
S_1	S_0	110